

Use **Data Flow Modeling** and write the codes of half subtractor and full subtractor (3-bits input and 2-bits output).

1. In the **module** file use **assign** statement
2. Write the testbench
3. Use RTL viewer and show the drawing of half subtractor and full subtractor
4. Simulate the testbench and make the analyze of timing diagram
5. Run the codes on the board